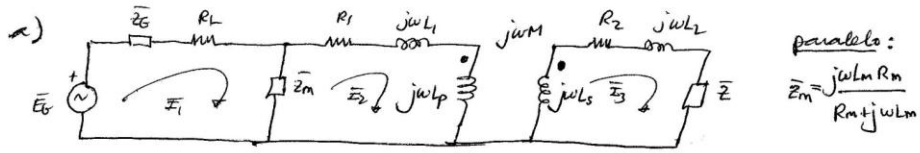


Junio 2008




paralelo:  

$$\bar{Z}_m = \frac{j\omega L_m R_m}{R_m + j\omega L_m}$$

$$\begin{aligned} \bar{E}_G &= (\bar{Z}_G + R_L + \bar{Z}_m) \bar{I}_1 - \bar{Z}_m \bar{I}_2 \\ 0 &= (R_1 + j\omega L_1 + j\omega L_2 + \bar{Z}_m) \bar{I}_2 - \bar{Z}_m \bar{I}_1 - j\omega M \bar{I}_3 \\ 0 &= (R_2 + j\omega L_2 + \bar{Z} + j\omega L_3) \bar{I}_3 - j\omega M \bar{I}_2 \end{aligned} \Rightarrow \begin{pmatrix} \bar{E}_G \\ 0 \\ 0 \end{pmatrix} = \begin{pmatrix} \bar{Z}_G + \bar{Z}_m + R_L & -\bar{Z}_m & 0 \\ -\bar{Z}_m & R_1 + \bar{Z}_m + j\omega L_1 + j\omega L_2 & -j\omega M \\ 0 & -j\omega M & R_2 + j\omega L_2 + \bar{Z} + j\omega L_3 \end{pmatrix} \begin{pmatrix} \bar{I}_1 \\ \bar{I}_2 \\ \bar{I}_3 \end{pmatrix}$$

Forma Matricial!

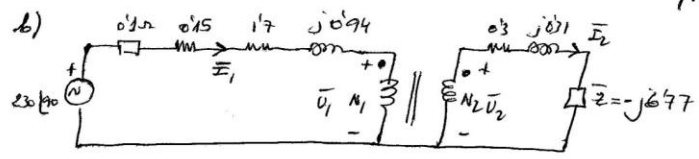

$\frac{N_1}{N_2} = 10$   
 $j\omega L_1 = j100\pi \cdot 30 = j0.94$   
 $j\omega L_2 = j100\pi \cdot 10^3 = j0.31$   
 $\bar{Z} = \frac{1}{j\omega C} = j \frac{1}{1000 \cdot 1000\pi} = -j6.77$

T.I.:  $\frac{U_1}{N_1} = \frac{U_2}{N_2} \rightarrow U_1 = 10 U_2$   
 $N_1 I_1 - N_2 I_2 = 0 \rightarrow I_1 = \frac{1}{10} I_2$


$\bar{Z} = 1k$   
 $j230 = 0.15 + 17 + j0.94 I_1 + U_1$   
 $0 = 10.3 + j0.31 - j6.77 I_2 - U_2$

$$\Rightarrow \begin{pmatrix} 230 \angle 0^\circ \\ 0 \\ 0 \end{pmatrix} = \begin{pmatrix} 17.15 + j0.94 & 10 \\ 3 - j6.46 & -1 \end{pmatrix} \begin{pmatrix} \bar{I}_1 \\ \bar{I}_2 \end{pmatrix}$$

$\bar{I}_1 = 0.356 \angle 177.16^\circ \text{ A}$

luego  $\bar{I}_2 = 10 \bar{I}_1 = 3.56 \angle 177.16^\circ \text{ A}$   
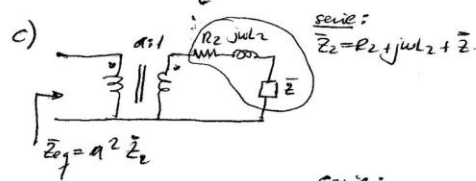
$$i(t) = 3.56 \sqrt{2} \cos(100\pi t + 177.16 \frac{\pi}{180}) \text{ A}$$



serie:  
 $\bar{Z}_2 = R_2 + j\omega L_2 + \bar{Z}$

serie:  
 $\bar{Z}_1 = R_1 + j\omega L_1 + a^2 \bar{Z}_2 = R_1 + j\omega L_1 + a^2 (R_2 + j\omega L_2 + \bar{Z})$   
 $\bar{Z}_1 = R_1 + a^2 R_2 + j\omega (L_1 + a^2 L_2) + a^2 \bar{Z}$

simplificada

Como queremos  $\cos\phi = 1$  (equivalente a  $\phi_{AB} = 0$ )  
 la parte imaginaria debería ser nula (de  $\bar{Z}_1$ )  

$$j\omega (L_1 + a^2 L_2) + a^2 \bar{Z} = 0 \rightarrow \bar{Z} = -j\omega \left( \frac{L_1}{a^2} + L_2 \right)$$

Sejio Cadizora Ibañez Sol.